LM2611 Demoboard

National Semiconductor Application Note 1203 Mark Hartman August 2001

.M2611 Demoboard

Introduction

The LM2611 demoboard is a working demonstration of a typical LM2611 Cuk converter layout. This application note contains information about the board. See the datasheet for more information on the LM2611 and Cuk topology.

General Description

The LM2611 is typically used in inverting Cuk converter applications. The Cuk converter offers the advantages of low input and output ripple current and the ability to step up or step down the magnitude of the input voltage. The NFB pin allows for simple feedback of the negative output voltage. The demoboard is assembled to show a small yet practical layout. The board will operate under the following conditions:



Note: The input capacitor is rated for 6.3V. Do not apply greater than 5.5V without first replacing the input capacitor with one of higher voltage rating ($V_{IN(MAX)} = 14V$). The input voltage may be as low as 2.7V, however the maximum load will be lower than 300 mA.



FIGURE 1.

TABLE 1. Bill of Materials

Component	Value	Description	Model Number
C _{BYP}	0.1µF	Bypass Capacitor	VJ0805Y104KXAAT (Vishay)
С _{сик}	2.2µF	Cuk Capacitor	EMK316BJ225ML (Taiyo
			Yuden)
C _{FF}	1nF	Feedforward Capacitor	VJ0805Y102KXAAT (Vishay)
C _{IN}	22µF/6.3V	Input Capacitor	LMK325BJ226MM (Taiyo
			Yuden)
C _{OUT}	22µF/6.3V	Output Capacitor	LMK325BJ226MM (Taiyo
			Yuden)
D		Scottky Diode	MBRM120LT3 (Motorola)
L ₁	22µH	Input Inductor	CR32-220 (Sumida)
L ₂	22µH	Output Inductor	CR32-220 (Sumida)
R _{FB1}	29.4kΩ	Feedback Resistor	CRCW08052492FRT1
			(Vishay)
R _{FB2}	10.0kΩ	Feedback Resistor	CRCW08051002FRT1
			(Vishay)







FIGURE 3. LM2611 Demoboard Bottom Layer Layout

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- 1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

AN-1203

National Semiconductor National Semiconductor Corporation Europe Americas Email: support@nsc.com www.national.com

Fax: +49 (0) 180-530 85 86 Email: europe.support@nsc.com Deutsch Tel: +49 (0) 69 9508 6208 English Tel: +44 (0) 870 24 0 2171 Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Response Group Tel: 65-2544466 Fax: 65-2504466 Email: ap.support@nsc.com National Semiconductor Japan Ltd. Tel: 81-3-5639-7560 Fax: 81-3-5639-7507

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.