

LM2694 Evaluation Board

National Semiconductor
Application Note 1472
Dennis Morgan
May 2006




Introduction

The LM2694EVAL evaluation board provides the design engineer with a fully functional buck regulator, employing the constant on-time (COT) operating principle. This evaluation board provides a 5V output over an input range of 8V - 30V. The circuit delivers load currents to 0.5A, with current limit set at $\approx 0.65A$. The board is populated with all external components except R4, C6, C9 and C12. These components provide options for managing the output ripple voltage as described later in this document.

The board's specification are:

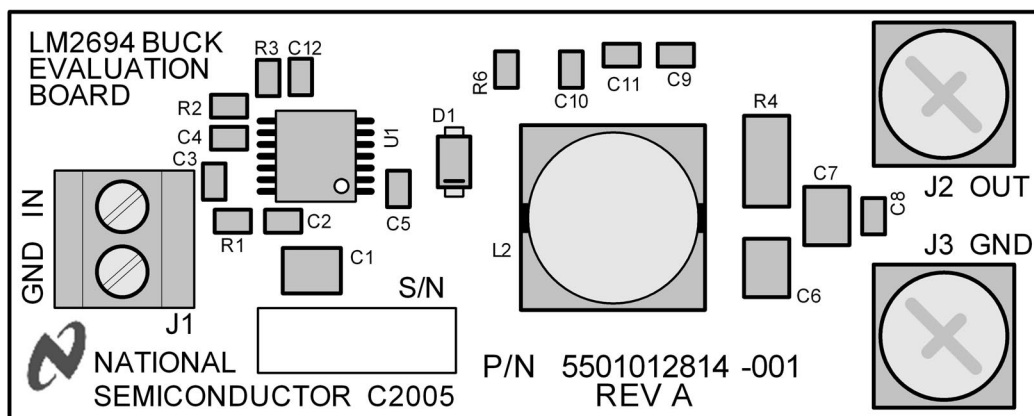- Input Voltage: 8V to 30V
- Output Voltage: 5V
- Maximum load current: 0.5A
- Minimum load current: 0A
- Current Limit: 0.65A
- Measured Efficiency: 93.4% ($V_{IN} = 8V$, $I_{OUT} = 200\text{ mA}$)
- Nominal Switching Frequency: 250 kHz
- Size: 2.25 in. x 0.88 in. x 0.55 in



20192001

FIGURE 1. Evaluation Board - Top Side

Theory of Operation

Refer to the evaluation board schematic in Figure 5. When the circuit is in regulation, the buck switch is on each cycle for a time determined by R1 and V_{IN} according to the equation:

$$t_{ON} = \frac{1.14 \times 10^{-10} \times (R1 + 1.4k)}{(V_{IN} - 1.5V)} + 95\text{ ns}$$

The on-time of this evaluation board ranges from $\approx 2600\text{ ns}$ at $V_{IN} = 8V$, to $\approx 660\text{ ns}$ at $V_{IN} = 30V$. The on-time varies inversely with V_{IN} to maintain a nearly constant switching frequency. At the end of each on-time the Minimum Off-Timer ensures the buck switch is off for at least 265 ns. In normal operation, the off-time is much longer. During the off-time, the output capacitor (C7) is discharged by the load current. When the output voltage falls sufficiently that the voltage at FB is below 2.5V, the regulation comparator initiates a new on-time period. For stable, fixed frequency operation, $\approx 25\text{ mV}$ of ripple is required at FB to switch the

regulation comparator. Refer to the LM2694 data sheet for a detailed block diagram, and a complete description of the various functional blocks.

Board Layout and Probing

The pictorial in Figure 1 shows the placement of the circuit components. The following should be kept in mind when the board is powered:

- 1) When operating at high input voltage and high load current, forced air flow is recommended.
- 2) The LM2694, and diode D1 may be hot to the touch when operating at high input voltage and high load current.
- 3) Use CAUTION when probing the circuit at high input voltages to prevent injury, as well as possible damage to the circuit.
- 4) At maximum load current (0.5A), the wire size and length used to connect the load becomes important. Ensure there is not a significant drop in the wires between this evaluation board and the load.

Board Connection/Start-up

The input connections are made to the J1 connector. The load is connected to the OUT and GND terminals. Ensure the wires are adequately sized for the intended load current. Before start-up a voltmeter should be connected to the input terminals, and to the output terminals. The load current should be monitored with an ammeter or a current probe. It is recommended that the input voltage be increased gradually to 8V, at which time the output voltage should be 5V. If the output voltage is correct with 8V at V_{IN} , then increase the input voltage as desired and proceed with evaluating the circuit.

Output Ripple Control

The LM2694 requires a minimum of 25 mVp-p ripple at the FB pin, in phase with the switching waveform at the SW pin, for proper operation. In the simplest configuration (Figure 4) that ripple is derived from the ripple at the output, generated by the inductor's ripple current flowing through R4. That ripple voltage is attenuated by the feedback resistors, requiring that the ripple amplitude at OUT be higher than the minimum of 25 mVp-p by the gain factor. Options for reducing the output ripple are discussed below, and the results are shown in the graph of Figure 8.

A) Minimum Output Ripple: This evaluation board is supplied configured for minimum ripple at OUT. The output ripple, which ranges from 2mVp-p at $V_{IN} = 8V$ to 3 mVp-p at $V_{IN} = 30V$, is determined primarily by the ESR of output capacitor (C7), and the inductor's ripple current, which ranges from 60 mA p-p to 100 mA p-p over the input voltage range. The ripple voltage required by the FB pin is generated by R6, C10 and C11 since the SW pin switches from -1V to

V_{IN} , and the right end of C10 is a virtual ground. The values for R6 and C10 are chosen to generate a 30-40 mVp-p triangle waveform at their junction. That triangle wave is then coupled to the FB pin through C11. The following procedure is used to calculate values for R6, C10 and C11:

1) Calculate the voltage V_A :

$$V_A = V_{OUT} - (V_{SW} \times (1 - (V_{OUT}/V_{IN})))$$

where V_{SW} is the absolute value of the voltage at the SW pin during the off-time (typically 1V), and V_{IN} is the minimum input voltage. For this circuit V_A calculates to 4.63V. This is the DC voltage at the R6/C10 junction, and is used in the next equation.


2) Calculate the R6 x C10 product:

$$R6 \times C10 = \frac{(V_{IN} - V_A) \times t_{ON}}{\Delta V}$$

where t_{ON} is the maximum on-time (≈ 2600 ns), V_{IN} is the minimum input voltage, and ΔV is the desired ripple amplitude at the R6/C10 junction, 30 mVp-p for this example.

$$R6 \times C10 = \frac{(8V - 4.63V) \times 2600 \text{ ns}}{0.03V} = 2.9 \times 10^{-4}$$

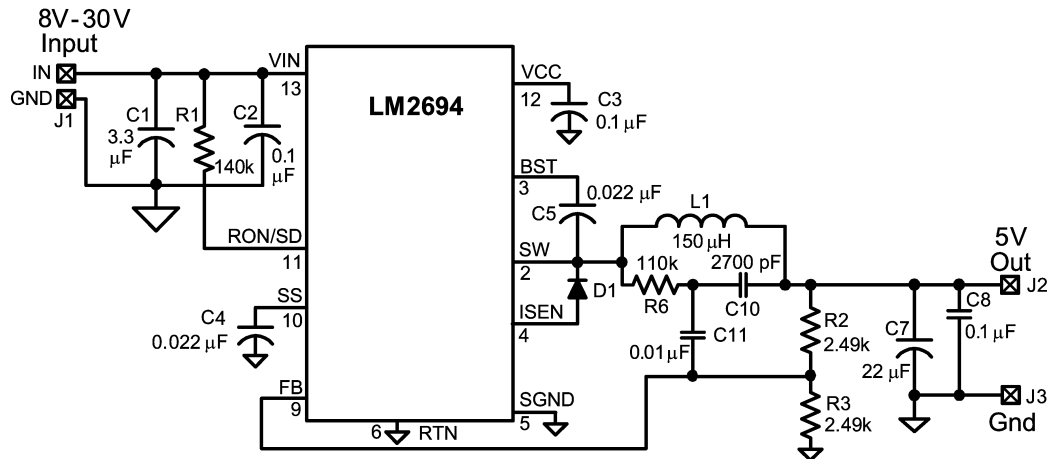R6 and C10 are then chosen from standard value components to satisfy the above product. For example, C10 can be 2700 pF requiring R6 to be 110 k Ω . C11 is chosen to be 0.01 μ F, large compared to C10. The circuit as supplied on this EVB is shown in Figure 2.



20192005

FIGURE 2. Minimum Output Ripple Configuration

B) Intermediate Ripple Level Configuration: This configuration generates more ripple at the output than the above configuration, but uses one less capacitor. If some ripple can

be tolerated in the application, this configuration is slightly more economical, and simpler. R4 and C6 and C9 are used instead of R6, C7, C8, C10 and C11, as shown in Figure 3.

Output Ripple Control (Continued)

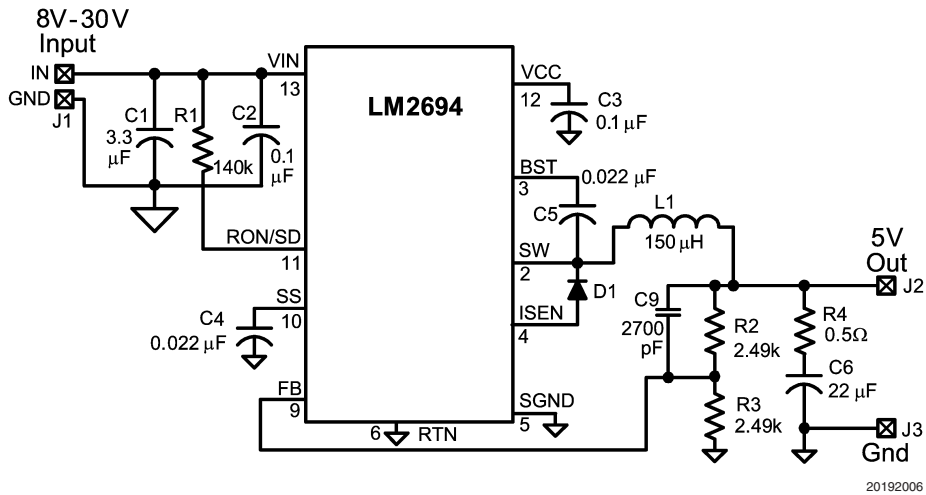


FIGURE 3. Intermediate Ripple Configuration

R4 is chosen to generate ≥ 25 mV - 30 mVp-p at the output, knowing that the minimum ripple current in this circuit is 60 mA-p-p at minimum V_{IN} . C9 couples that ripple to the FB pin without the attenuation of the feedback resistors. C9's minimum value is calculated from:

$$C9 = \frac{t_{ON(max)}}{(R2//R3)}$$

where $t_{ON(max)}$ is the maximum on-time (at minimum V_{IN}), and $R2//R3$ is the equivalent parallel value of the feedback resistors. For this evaluation board $t_{ON(max)}$ is approximately 2600 ns, and $R2//R3 = 1.25$ k Ω , and C9 calculates to a minimum of 2080 pF. The resulting ripple at the output ranges from 30 mVp-p to 50 mVp-p over the input voltage range.

C) **Lowest Cost Configuration:** This configuration is the same as option B above, but without C9. Since 25 mVp-p are required at the FB pin, R4 is chosen to generate 50 mV at OUT, knowing that the minimum ripple current in this circuit is 60 mA-p-p at minimum V_{IN} . To allow for tolerances, 1.0 Ω is used for R4. The resulting ripple at OUT ranges from ≈ 60 mVp-p to ≈ 100 mVp-p over the input voltage range. If the application can tolerate this ripple level, this is the most economical solution. The circuit is shown in Figure 4. An alternative to this circuit is to eliminate R4 if C6 has sufficient ESR.

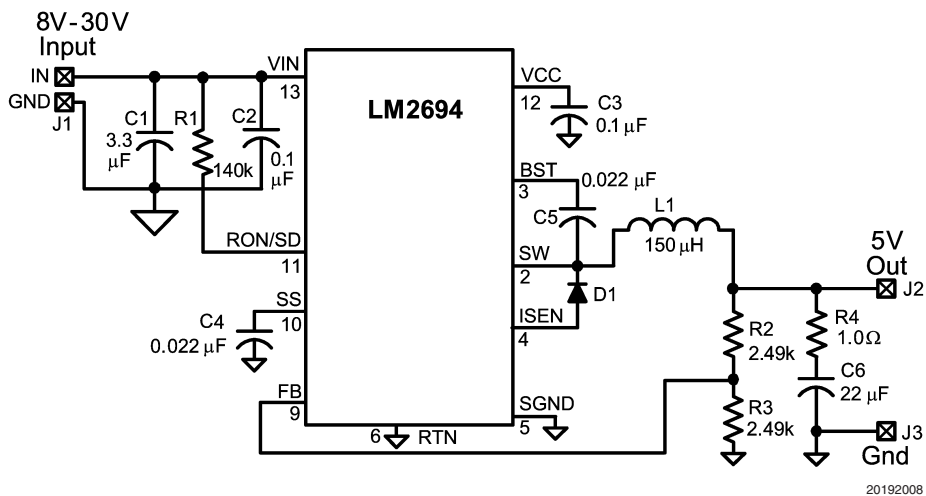


FIGURE 4. Lowest Cost Configuration


Minimum Load Current

The LM2694 requires a minimum load current of $\approx 500 \mu\text{A}$ to ensure the boost capacitor (C5) is recharged sufficiently during each off-time. In this evaluation board, the minimum load current is provided by the feedback resistor (R2, R3), allowing the board's minimum load current to be specified at zero.

Circuit Performance

Figures 6 through 9 indicate the performance of this evaluation board. Figure 10 indicates waveforms at various points

within the circuit, and Figure 11 indicates how the output responds to the load current changing between 200 mA and 400 mA. Figure 12 indicates the preferred method for using a scope probe to measure output ripple and transient waveforms. The probe's ground ring touches the output ground terminal (J3) and the probe's tip touches the 5V output terminal (J2). This method eliminates noise and switching spikes which the probe's ground lead would pick up if it were used.

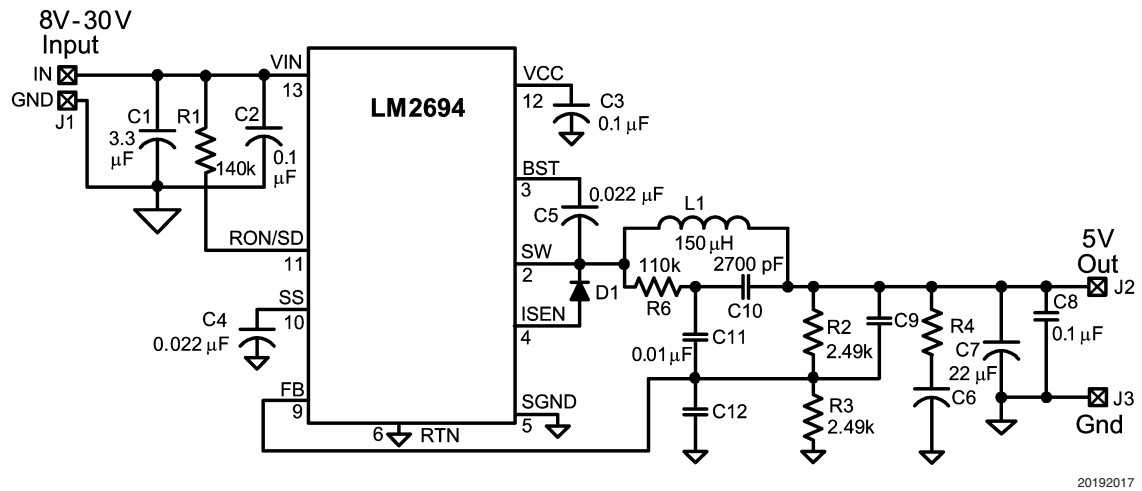


20192017

FIGURE 5. Evaluation Board Schematic


Item	Description	Mfg., Part Number	Package	Value
C1	Ceramic Capacitor	TDK C3225X7R1H335M	1210	3.3 μF , 50V
C2, 3, 8	Ceramic Capacitor	TDK C2012X7R2A104M	0805	0.1 μF , 100V
C4, 5	Ceramic Capacitor	TDK C2012X7R2A223M	0805	0.022 μF , 100V
C6		Unpopulated	1210	
C7	Ceramic Capacitor	TDK C3225X7R1C226M	1210	22 μF , 16V
C9		Unpopulated	0805	
C10	Ceramic Capacitor	TDK C2012X7R2A272M	0805	2700 pF, 100V
C11	Ceramic Capacitor	TDK C2012X7R2A103M	0805	0.01 μF , 100V
C12	Ceramic Capacitor	Unpopulated	0805	
D1	Schottky Diode	Diodes Inc. DFSL160	Power DI 123	60V, 1A
L1	Inductor	TDK SLF10145-151MR79, or Cooper Bussman DR74-151	10 mm x 10 mm	150 μH , 0.8A
R1	Resistor	Vishay CRCW08051413F	0805	140k Ω
R2, R3	Resistor	Vishay CRCW08052491F	0805	2.49k Ω
R4	Resistor	Unpopulated	2010	
R6	Resistor	Vishay CRCW08051103F	0805	110k Ω
U1	Switching Regulator	National Semiconductor LM2694MT	TSSOP-14	

Circuit Performance

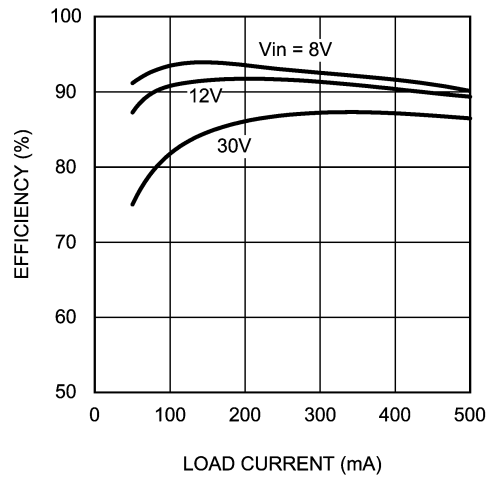

20192018


FIGURE 6. Efficiency vs Load Current

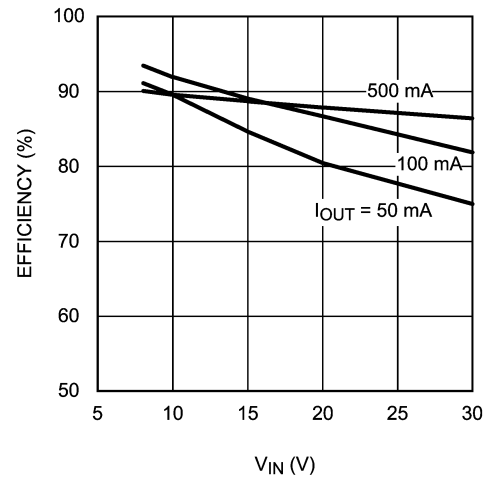

20192019


FIGURE 7. Efficiency vs Input Voltage

Circuit Performance (Continued)

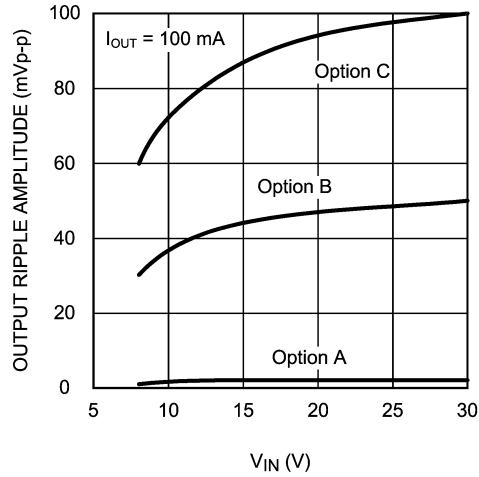


20192020

FIGURE 8. Output Voltage Ripple

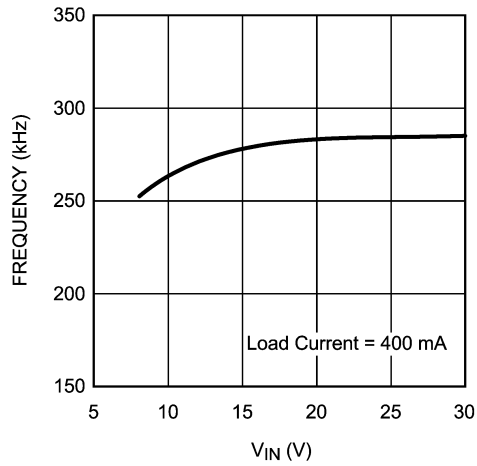

20192021


FIGURE 9. Switching Frequency vs. Input Voltage

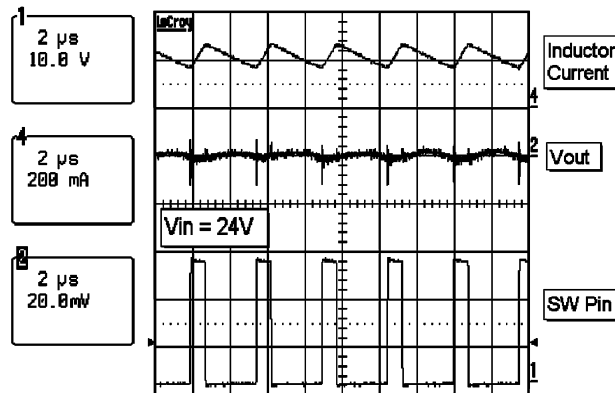

20192025


FIGURE 10. Circuit Waveforms

Circuit Performance (Continued)

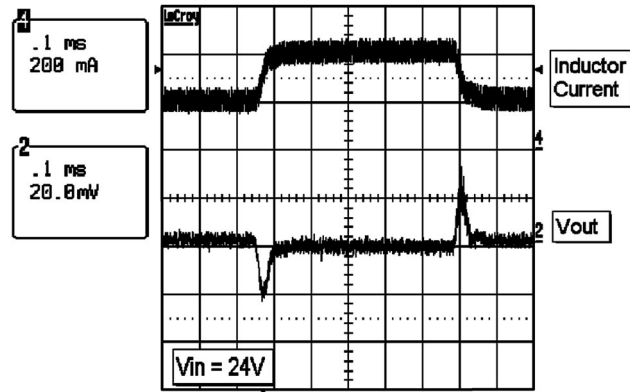

20192026


FIGURE 11. Transient Response

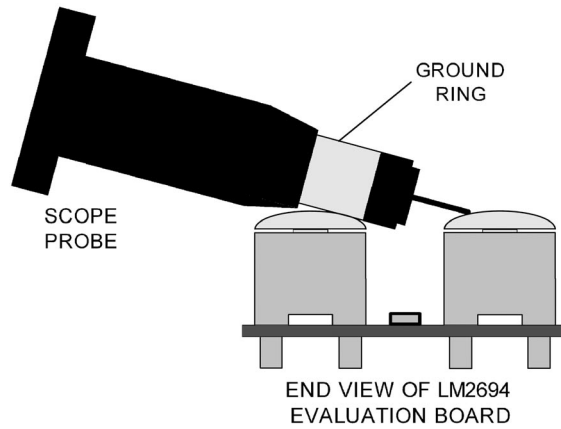

20192027


FIGURE 12. Preferred Method for Measuring Output Waveforms

PCB Layout

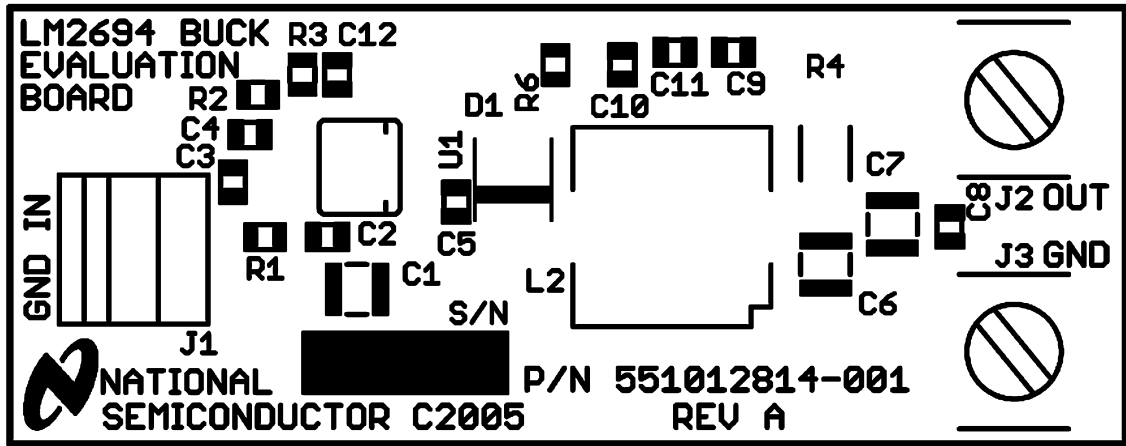


Board Silkscreen

20192022

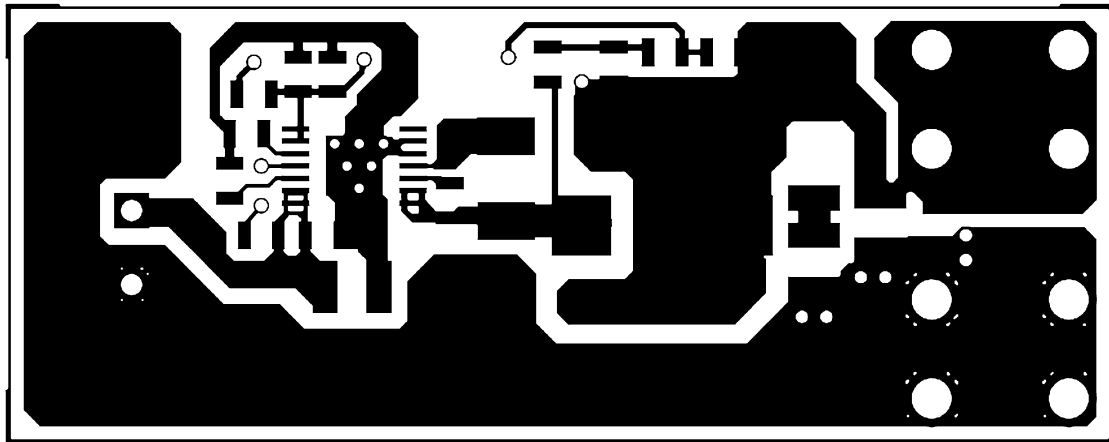

Board Top Layer

20192023

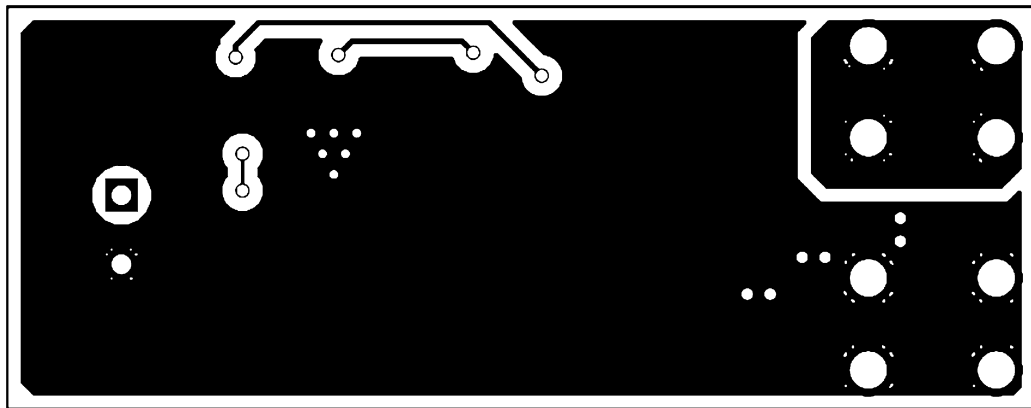

Board Bottom Layer (viewed from top)

20192024

Notes

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor manufactures products and uses packing materials that meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959

www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560