LM2717 Evaluation Board

National Semiconductor Application Note 1371 Clinton Jensen October 2005




Introduction


The LM2717 is composed of two high current PWM DC/DC buck converters. The first buck (step-down) converter provides a fixed 3.3V output at up to 1.5A. The second buck converter provides an adjustable output at up to 2A. The LM2717 evaluation board is designed for 3.3V output at up to 1.5A and 5V output up to 2A with an input voltage range of 8V to 20V. The board is ideally set up for converting a

standard 12V rail to 3.3V and 5V found in many applications. The 5V output may be changed to fit other applications as desired. The LM2717 is also ideal for TFT applications with high input voltages. It can convert an 18V to 20V source to 3.3V for the control circuitry and 8V to 15V for the panel bias voltage. The schematic, layout, and bill of materials used follows:

Schematic and Layout

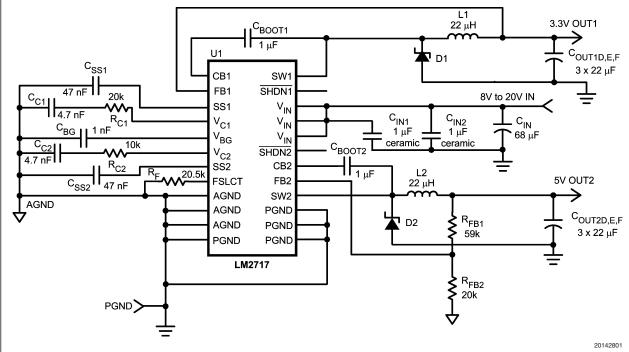


Schematic and Layout (Continued)

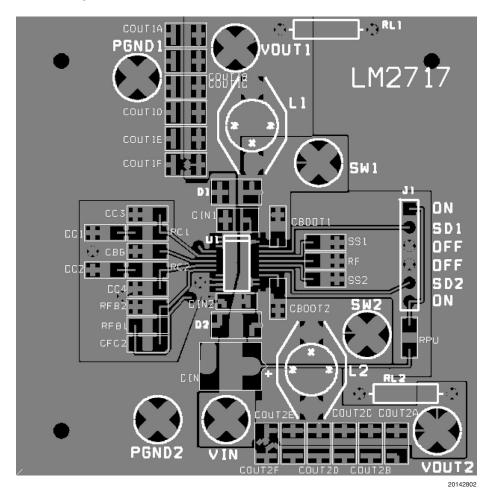

Layout, Top Layer

www.national.com 2

Schematic and Layout (Continued)

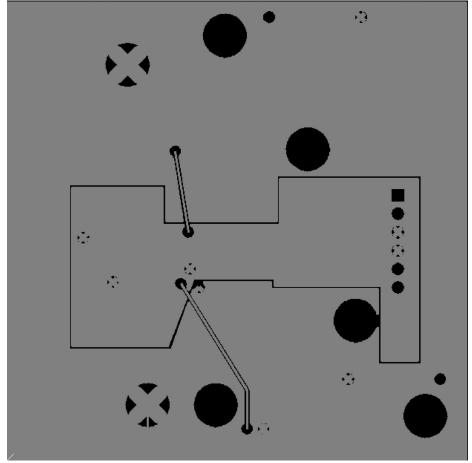

Layout, Bottom Layer

20142803

Bill of Materials

Designator	Component	Manufacturer
U1	LM2717MT, TSSOP-24	National Semiconductor
L1, L2	22 μH, DO3316P-223	Coilcraft
C _{IN}	68 μF, 20V Tantalum, 595D686X9025R	Vishay
C _{IN1} , C _{IN2} , C _{BOOT1} , C _{BOOT2}	1 μF, Ceramic, LMK316BJ105ML	Taiyo Yuden
C _{OUT1D} , C _{OUT1E} , C _{OUT1F} , C _{OUT2D} , C _{OUT2E} , C _{OUT2F}	22 μF, 6.3V Ceramic, LMK325BJ226MM	Taiyo Yuden
D1, D2	2A, 40V Schottky, MBRS240LT	On Semiconductor
C _{C1} , C _{C2}	4.7 nF, 1206 Case, VJ1206A472KXAA	Vishay
C_{BG}	1 nF, 1206 Case, VJ1206A102KXAA	Vishay
C _{C3} , C _{C4}	Open	
C _{SS1} , C _{SS2}	Open	
R _{C1} , R _{FB2}	20k, 1206 Case, CRCW12062002F	Vishay
R _{C2}	10k, 1206 Case, CRCW12061002F	Vishay
R _F	20.5k, 1206 Case, CRCW12062052F	Vishay
RPU	100k, 1206 Case, CRCW12061003F	Vishay
R _{FB1}	59k, 1206 Case, CRCW12065902F	Vishay
Test Posts (7)	160-2141-02-01-00	Cambion

3 www.national.com

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

Notes

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor manufactures products and uses packing materials that meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



National Semiconductor Americas Customer Support Center

Email: new.feedback@nsc.com Tel: 1-800-272-9959

www.national.com

National Semiconductor Europe Customer Support Center Fax: +49 (0) 180-530 85 86

Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Support Center Email: ap.support@nsc.com National Semiconductor Japan Customer Support Center Fax: 81-3-5639-7507 Email: jpn.feedback@nsc.com Tel: 81-3-5639-7560