

LM34930 Evaluation Board

National Semiconductor
Application Note 1848
Dennis Morgan
April 29, 2008




Introduction

The LM34930EVAL evaluation board provides the design engineer with a fully functional buck regulator, employing the constant on-time (COT) operating principle. This evaluation board provides a 5V output over an input range of 8V to 33V. The circuit delivers load currents to 1A, with current limit set at a nominal 1.16A. The board is populated with all components except R5, C9 and C10. These components provide options for managing the output ripple as described later in this document.

The board's specification are:

 - Input Voltage: 8V to 33V
- Output Voltage: 5V
- Maximum load current: 1A
- Minimum load current: 0A
- Current Limit: 1.14A to 1.19A
- Measured Efficiency: 92.2% ($V_{IN} = 8V$, $I_{OUT} = 400\text{ mA}$)
- Nominal Switching Frequency: 1500 kHz
- Size: 2.6 in. x 1.6 in. x 0.5 in



Note: R2, C3, C4, C9 and C11 are located on board's back side.

30063001

FIGURE 1. Evaluation Board - Top Side

Theory of Operation

Refer to the evaluation board schematic in *Figure 5*. When the circuit is in regulation, the buck switch is on each cycle for a time determined by R1 and V_{IN} according to the equation:

$$t_{ON} = \frac{4.15 \times 10^{-11} \times (R1 + 0.5\text{ k}\Omega)}{V_{IN} - 0.8V} + 65\text{ ns}$$

The on-time of this evaluation board ranges from $\approx 416\text{ ns}$ at $V_{IN} = 8V$, to $\approx 144\text{ ns}$ at $V_{IN} = 33V$. The on-time varies inversely with V_{IN} to maintain a nearly constant switching fre-

quency. At the end of each on-time the Minimum Off-Timer ensures the buck switch is off for at least 90 ns. In normal operation, the off-time is much longer. During the off-time, the load current is supplied by the output capacitor (C7, C8). When the output voltage falls sufficiently that the voltage at FB is below 2.52V, the regulation comparator initiates a new on-time period. For stable, fixed frequency operation, a minimum of 25 mV of ripple is required at FB to switch the regulation comparator. The current limit threshold, is $\approx 1.19A$ at $V_{in} = 8V$, and $\approx 1.14A$ at $V_{in} = 33V$. Refer to the LM34930 data sheet for a more detailed block diagram, and a complete description of the various functional blocks.

Board Layout and Probing

The pictorial in *Figure 1* shows the placement of the circuit components. The following should be kept in mind when the board is powered:

- 1) When operating at high input voltage and high load current, forced air flow may be necessary.
- 2) The LM34930, and diode D1 may be hot to the touch when operating at high input voltage and high load current.
- 3) Use CAUTION when probing the circuit at high input voltages to prevent injury, as well as possible damage to the circuit.
- 4) At maximum load current (1A), the wire size and length used to connect the load becomes important. Ensure there is not a significant drop in the wires between this evaluation board and the load.

Board Connection/Start-up

The input connections are made to the J1 connector. The load is connected to the J2 (OUT) and J3 (GND) terminals. Ensure the wires are adequately sized for the intended load current. Before start-up a voltmeter should be connected to the input terminals, and to the output terminals. The load current should be monitored with an ammeter or a current probe. It is rec-

ommended that the input voltage be increased gradually to 8V, at which time the output voltage should be 5V. If the output voltage is correct with 8V at V_{IN} , then increase the input voltage as desired and proceed with evaluating the circuit. DO NOT EXCEED 40V AT V_{IN} .

Output Ripple Control

The LM34930 requires a minimum of 25 mVp-p ripple at the FB pin, in phase with the switching waveform at the SW pin, for proper operation. The required ripple can be supplied from ripple at V_{OUT} , through the feedback resistors as described in Options A and B below, or the ripple can be generated separately (using R5, C9, and C10) in order to keep the ripple at V_{OUT} at a minimum (Option C).

Option A) Lowest Cost Configuration: In this configuration R4 is installed in series with the output capacitance (C7, C8). Since ≥ 25 mVp-p are required at the FB pin, R4 must be chosen to generate ≥ 50 mVp-p at V_{OUT} , knowing that the minimum ripple current in this circuit is ≈ 125 mA p-p at minimum V_{IN} . Using 0.43Ω for R4, the ripple at V_{OUT} ranges from ≈ 54 mVp-p to ≈ 160 mVp-p over the input voltage range. If the application can accept this ripple level, this is the most economical solution. The circuit is shown in *Figure 2*. See *Figure 8*.

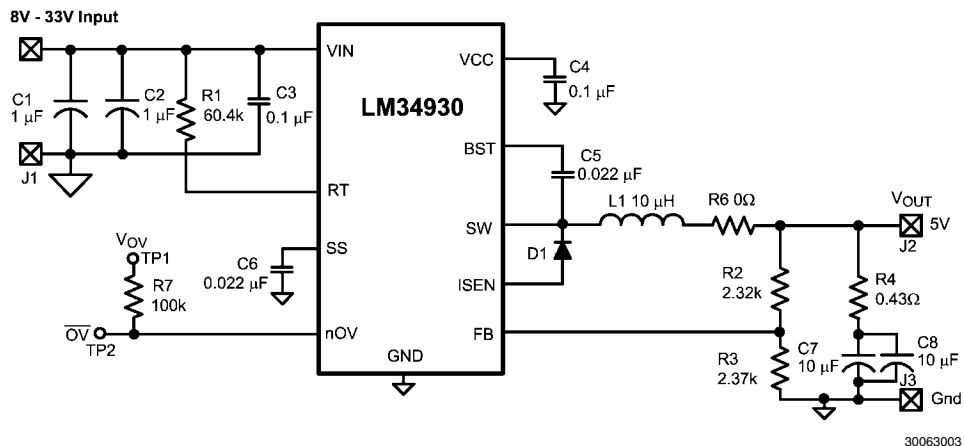


FIGURE 2. Lowest Cost Configuration

Option B) Intermediate Ripple Configuration: This evaluation board is supplied with this configuration installed. This configuration generates less ripple at V_{OUT} than option A

above by the addition of one capacitor (C11) across R2, as shown in *Figure 3*.

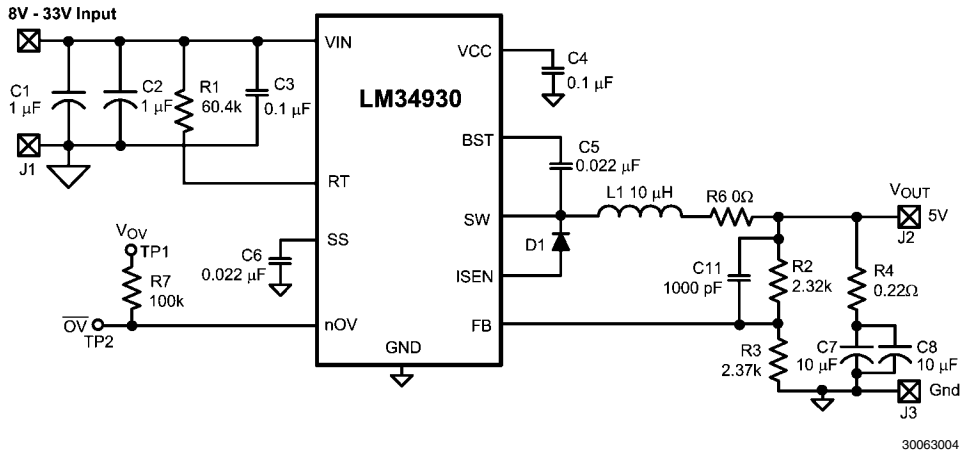


FIGURE 3. Intermediate Ripple Configuration

Since the output ripple is passed by Cff to the FB pin with little or no attenuation, R4 can be reduced so the minimum ripple at V_{OUT} is ≈25 mVp-p. The minimum value for Cff is calculated from:

$$C_{ff} \geq \frac{3 \times t_{ON(max)}}{(R2//R3)}$$

where t_{ON(max)} is the maximum on-time (at minimum V_{IN}), and R2//R3 is the parallel equivalent of the feedback resistors. The ripple at V_{OUT} ranges from 32 mVp-p to 93 mVp-p over the input voltage range. See Figure 8.

Option C) Minimum Ripple Configuration: To obtain minimum ripple at V_{OUT}, R4 is set to 0Ω, and R5, C9, and C10 are added to generate the required ripple for the FB pin. In this configuration, the output ripple is determined primarily by the characteristics of the output capacitance and the inductor's ripple current. See Figure 4.

The ripple voltage required by the FB pin is generated by R5, C10, and C9 since the SW pin switches from -1V to V_{IN}, and the right end of C10 is a virtual ground. The values for R5 and C10 are chosen to generate a 50-100 mVp-p triangle waveform at their junction. That triangle wave is then coupled to the FB pin through C9. The following procedure is used to calculate values for R5, C10 and C9:

1) Calculate the voltage V_A:

$$V_A = V_{OUT} - (V_{SW} \times (1 - (V_{OUT}/V_{IN})))$$

where V_{SW} is the absolute value of the voltage at the SW pin during the off-time (typically 1V), and V_{IN} is the minimum input voltage. For this circuit, V_A calculates to 4.63V. This is the approximate DC voltage at the R5/C10 junction, and is used in the next equation.

2) Calculate the R5 x C10 product:

$$R5 \times C10 = \frac{(V_{IN} - V_A) \times t_{ON}}{\Delta V}$$

where t_{ON} is the maximum on-time (≈416 ns), V_{IN} is the minimum input voltage, and ΔV is the desired ripple amplitude at the R5/C10 junction, 100 mVp-p for this example.

$$R5 \times C10 = \frac{(8V - 4.63V) \times 416 \text{ ns}}{0.1V} = 14 \times 10^{-6}$$

R5 and C10 are then chosen from standard value components to satisfy the above product. Typically C10 is 3000 to 10000 pF, and R5 is 10 kΩ to 300 kΩ. C9 is chosen large compared to C10, typically 0.1 μF. The ripple at V_{OUT} is typically less than 10 mVp-p. See Figure 4 and Figure 8.

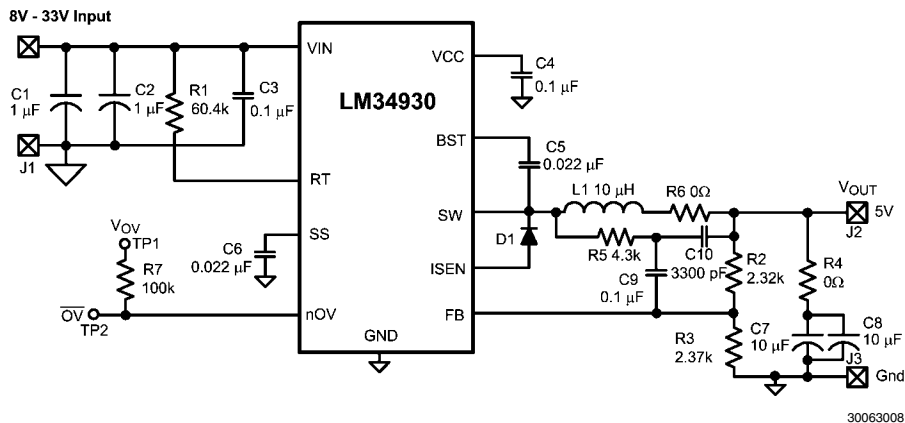


FIGURE 4. Minimum Output Ripple Configuration

Over-Voltage Indicator

The nOV pin, an open drain logic output, switches low when the voltage at VIN exceeds 19V. The over-voltage indicator comparator provides 1.95V hysteresis to reject noise and ripple on the VIN pin. A pull-up voltage not exceeding 7V must be connected to TP1. A 100 k Ω pull-up resistor (R7) is provided on this board. The state of the nOV pin can be monitored at TP2.

The pull-up voltage can exceed the voltage at VIN. When nOV is low, the current into the pin must not exceed 10 mA.

Input Over-Voltage Shutdown

If the input voltage at VIN increases above 36V an internal comparator disables the buck switch, and grounds the soft-start pin. The over-voltage shutdown comparator provides 400 mV hysteresis to reject noise and ripple on the VIN pin. Normal operation resumes when the voltage at VIN is reduced below the lower threshold.

Monitor The Inductor Current

The inductor's current can be monitored or viewed on a scope with a current probe. Remove R6, and install an appropriate current loop across the two large pads where R6 was located. In this way the inductor's ripple current and peak current can be accurately determined.

Scope Probe Adapters

Scope probe adapters are provided on this evaluation board for monitoring the waveform at the SW pin, and at the circuit's output (V_{OUT}), without using the probe's ground lead which can pick up noise from the switching waveforms. The probe adapters are suitable for Tektronix P6137 or similar probes, with a 0.135" diameter.

Minimum Load Current

The LM34930 requires a minimum load current of ≈ 1 mA to ensure the boost capacitor (C5) is recharged sufficiently during each off-time. In this evaluation board, the minimum load current is provided by the feedback resistors allowing the board's minimum load current at V_{OUT} to be specified at zero.


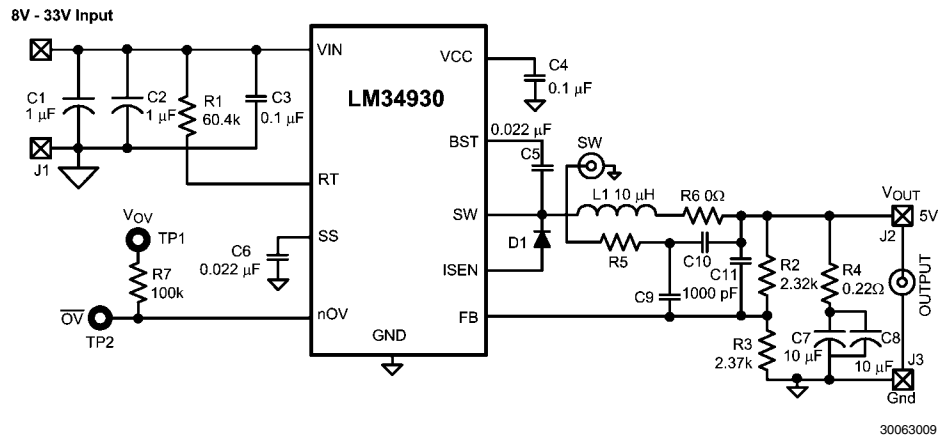


FIGURE 5. Complete Evaluation Board Schematic (As Supplied)

Bill of Materials


Item	Description	Mfg., Part Number	Package	Value
C1	Ceramic Capacitor	TDK C3216X7R1H105M	1206	1.0 μ F, 50V
C2	Ceramic Capacitor	TDK C3216X7R1H105M	1206	1.0 μ F, 50V
C3	Ceramic Capacitor	TDK C1608X7R1H104K	0603	0.1 μ F, 50V
C4	Ceramic Capacitor	TDK C1608X7R1H104K	0603	0.1 μ F, 50V
C5	Ceramic Capacitor	TDK C1608X7R1H223K	0603	0.022 μ F, 50V
C6	Ceramic Capacitor	TDK C1608X7R1H223K	0603	0.022 μ F, 50V
C7, C8	Ceramic Capacitor	TDK C3216X7R1C106K	1206	10 μ F, 16V
C9	Ceramic Capacitor	Unpopulated	0603	
C10	Ceramic Capacitor	Unpopulated	0603	
C11	Ceramic Capacitor	TDK C1608X7R2A102M	0603	1000 pF
D1	Schottky Diode	Zetex ZLLS2000	SOT23-6	40V, 2.2A
L1	Power Inductor	Bussman DR73-100	7.6 mm x 7.6 mm	10 μ H, 2A
R1	Resistor	Vishay CRCW06036042F	0603	60.4 k Ω
R2	Resistor	Vishay CRCW06032321F	0603	2.32 k Ω
R3	Resistor	Vishay CRCW06032371F	0603	2.37 k Ω
R4	Resistor	Panasonic ERJ3RQFR22	0603	0.22 Ω
R5	Resistor	Unpopulated	0603	
R6	Resistor	Vishay CRCW08050000Z	0805	0 Ω Jumper
R7	Resistor	Vishay CRCW06031003F	0603	100 k Ω
U1	Switching Regulator	National Semiconductor LM34930TL	12 Bump μ SMD	

Circuit Performance

 


30063010

FIGURE 6. Efficiency vs Load Current

 


30063011

FIGURE 7. Efficiency vs Input Voltage

 


30063012

FIGURE 8. Output Voltage Ripple

 

30063013


FIGURE 9. Switching Frequency vs. Input Voltage

 

30063014


FIGURE 10. Load Current Limit vs Input Voltage

Typical Waveforms

 

Trace 1 = SW Pin
 Trace 3 = V_{OUT}
 Trace 4 = Inductor Current
 $V_{in} = 16V$, $I_{out} = 400\text{ mA}$


FIGURE 11. Continuous Conduction Mode

 

Trace 1 = SW Pin
 Trace 3 = V_{OUT}
 Trace 4 = Inductor Current
 $V_{in} = 16V$, $I_{out} = 0\text{ mA}$


FIGURE 12. Discontinuous Conduction Mode

PC Board Layout

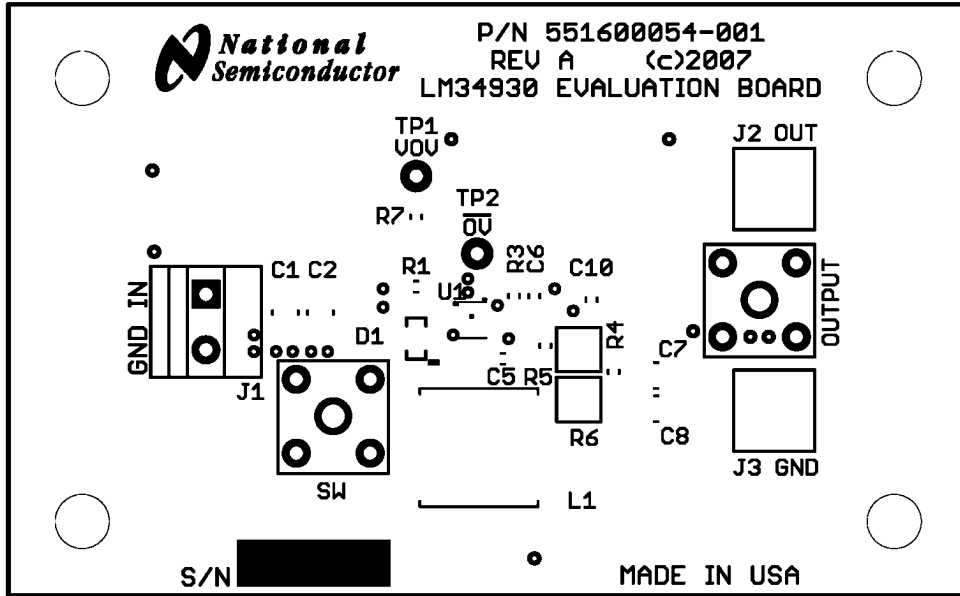


Board Silkscreen

30063017

 


Board Top Layer

30063018

 

Board Bottom Layer (Viewed from Top)

30063019

 

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH	www.national.com/webench
Audio	www.national.com/audio	Analog University	www.national.com/AU
Clock Conditioners	www.national.com/timing	App Notes	www.national.com/appnotes
Data Converters	www.national.com/adc	Distributors	www.national.com/contacts
Displays	www.national.com/displays	Green Compliance	www.national.com/quality/green
Ethernet	www.national.com/ethernet	Packaging	www.national.com/packaging
Interface	www.national.com/interface	Quality and Reliability	www.national.com/quality
LVDS	www.national.com/lvds	Reference Designs	www.national.com/refdesigns
Power Management	www.national.com/power	Feedback	www.national.com/feedback
Switching Regulators	www.national.com/switchers		
LDOs	www.national.com/lido		
LED Lighting	www.national.com/led		
PowerWise	www.national.com/powerwise		
Serial Digital Interface (SDI)	www.national.com/sdi		
Temperature Sensors	www.national.com/tempsensors		
Wireless (PLL/VCO)	www.national.com/wireless		

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation

For the most current product information visit us at www.national.com



**National Semiconductor
Americas Technical
Support Center**
Email:
new.feedback@nsc.com
Tel: 1-800-272-9959

**National Semiconductor Europe
Technical Support Center**
Email: europe.support@nsc.com
German Tel: +49 (0) 180 5010 771
English Tel: +44 (0) 870 850 4288

**National Semiconductor Asia
Pacific Technical Support Center**
Email: ap.support@nsc.com

**National Semiconductor Japan
Technical Support Center**
Email: jpn.feedback@nsc.com