

Wide Bandwidth OPERATIONAL TRANSCONDUCTANCE AMPLIFIER (OTA)

¹FEATURES

- •**Wide Bandwidth (80MHz, Open-Loop, G ⁼ +5)**
- **High Slew Rate (900V/µs)**
- •
- •**External IQ-Control**
- •**Low Quiescent Current (5.4mA)**

APPLICATIONS

- •
- •**Communications Equipment**
- •**High-Speed Data Acquisition**
- •
- **Control Loop Amplifiers**
- •**Wideband Active Filters**
- •

DESCRIPTION

The OPA861 is ^a versatile monolithic component designed for wide-bandwidth systems, including high performance video, RF and IF circuitry. The OPA861 is ^a wideband, bipolar operational transconductance amplifier (OTA).

The OTA or voltage-controlled current source can be viewed as an *ideal transistor*. Like ^a transistor, it has three terminals—a high impedance input (base), ^a low-impedance input/output (emitter), and the current **High Transconductance (95mA/V) but and the COLLECTOF COLLECTOF COLLECTION** COLLECTION COLLECTION **The COLLECTION** self-biased and bipolar. The output collector current is zero for ^a zero base-emitter voltage. AC inputs centered about zero produce an output current, which is bipolar and centered about zero. The transconductance of the OPA861 can be adjusted **Video/Broadcast Equipment** with an external resistor, allowing bandwidth, quiescent current, and gain trade-offs to be optimized.

Wideband LED Drivers Notation 2018 Used as a basic building block, the OPA861 simplifies the design of AGC amplifiers, LED driver circuits for fiber optic transmission, integrators for fast pulses, fast control loop amplifiers and control **Line Drivers Exercise 2.1 A.1 Strategiers amplifiers** for capacitive sensors, and active filters. The OPA861 is available in SO-8 and SOT23-6 surface-mount packages.

Low−Pass Negative Impedance Converter (NIC) Filter Frequency Response of 20kHz and 10MHz

Low−Pass NIC Filters

Please be aware that an important notice concerning availability, standard warranty, and use in critical applications of Texas Instruments semiconductor products and disclaimers thereto appears at the end of this data sheet.

SBOS338E–AUGUST 2005–REVISED AUGUST 2008.. **www.ti.com**

This integrated circuit can be damaged by ESD. Texas Instruments recommends that all integrated circuits be handled with appropriate precautions. Failure to observe proper handling and installation procedures can cause damage.

ESD damage can range from subtle performance degradation to complete device failure. Precision integrated circuits may be more susceptible to damage because very small parametric changes could cause the device not to meet its published specifications.

ORDERING INFORMATION(1)

(1) For the most current package and ordering information, see the Package Option Addendum at the end of this document, or see the TI web site at [www.ti.com](http://www-s.ti.com/sc/techlit/www.ti.com).

ABSOLUTE MAXIMUM RATINGS(1)

(1) Stresses above these ratings may cause permanent damage. Exposure to absolute maximum conditions for extended periods may degrade device reliability. These are stress ratings only, and functional operations of the device at these and any other conditions beyond those specified is not supported.

(2) Pin 2 for the SO-8 package > 500V HBM. Pin 4 for the SOT23-6 package > 500V HBM.

PIN CONFIGURATION

ELECTRICAL CHARACTERISTICS: $V_s = \pm 5V$

 $R_L = 500\Omega$ and $R_{ADJ} = 250\Omega$, unless otherwise noted.

(1) Test levels: (A) 100% tested at +25°C. Over temperature limits set by characterization and simulation. (B) Limits set by characterization and simulation. (C) Typical value only for information.

(2) Junction temperature = ambient for $+25^{\circ}$ C specifications.

(3) Junction temperature = ambient at low temperature limit; junction temperature = ambient + 7° C at high temperature limit for over temperature specifications.

(4) Current is considered positive out of node.

SBOS338E–AUGUST 2005–REVISED AUGUST 2008.. **www.ti.com**

ELECTRICAL CHARACTERISTICS: $V_s = \pm 5V$ **(continued)**

 R_L = 500Ω and R_{ADJ} = 250Ω, unless otherwise noted.

ELECTRICAL CHARACTERISTICS: $V_s = +5V$

 R_L = 500Ω to V_S/2 and R_{ADJ} = 250Ω, unless otherwise noted.

(1) Test levels: (A) 100% tested at +25°C. Over temperature limits set by characterization and simulation. (B) Limits set by characterization and simulation. (C) Typical value only for information.

(2) Junction temperature = ambient for $+25^{\circ}$ C specifications.

(3) Junction temperature = ambient at low temperature limit; junction temperature = ambient + 3° C at high temperature limit for over temperature specifications.

(4) Current is considered positive out of node.

SBOS338E–AUGUST 2005–REVISED AUGUST 2008.. **www.ti.com**

ELECTRICAL CHARACTERISTICS: $V_s = +5V$ **(continued)**

 R_L = 500Ω to V_S/2 and R_{ADJ} = 250Ω, unless otherwise noted.

EXAS NSTRUMENTS

www.ti.com **www.ticom** and the set of the set

TYPICAL CHARACTERISTICS: $V_s = \pm 5V$

At T_A = +25°C, I_Q = 5.4mA, and R_L = 500 Ω , unless otherwise noted.

TYPICAL CHARACTERISTICS: $V_s = \pm 5V$ **(continued)**

At T_A = +25°C, I_Q = 5.4mA, and R_L = 500Ω, unless otherwise noted.

www.ti.com.. SBOS338E–AUGUST 2005–REVISED AUGUST 2008

TYPICAL CHARACTERISTICS: $V_s = \pm 5V$ **(continued)**

At T_A = +25°C, I_Q = 5.4mA, and R_L = 500Ω, unless otherwise noted.

SBOS338E–AUGUST 2005–REVISED AUGUST 2008.. **www.ti.com**

XAS **NSTRUMENTS**

www.ti.com.. SBOS338E–AUGUST 2005–REVISED AUGUST 2008

TYPICAL CHARACTERISTICS: $V_s = +5V$ **(continued)**

At T_A = +25°C, I_Q = 4.7mA, and R_L = 500 Ω to V_S/2, unless otherwise noted.

APPLICATION INFORMATION

The OPA861 is a versatile monolithic transconductance amplifier designed for wide-bandwidth systems, including high-performance **OVERVIEW** video, RF, and IF circuitry. The operation of the The symbol for the OTA section is similar to a
OPA861 is discussed in the OTA (Operational transistor (see Figure 28). Applications circuits for the OPA861 is discussed in the *OTA (Operational* transistor (see Figure 28). Applications circuits for the *Transconductance Amplifier)* section of this data OTA look and operate much like transistor the OTA section of an op amp has been referred to current source. Not only does this characteristic
as a Diamond Transistor, Voltage-Controlled Current simplify the understanding of application circuits, it as a Diamond Transistor, Voltage-Controlled Current simplify the understanding of application circuits, it
source, Transconductor, Macro Transistor, or positive aids the circuit optimization process as well. Many of source, Transconductor, Macro Transistor, or positive aids the circuit optimization process as well. Many of second-generation current conveyor (CCII+). The same intuitive techniques used with transistor second-generation current conveyor (CCII+). the same intuitive techniques used with transistor Corresponding symbols for these terms are shown in designs apply to OTA circuits. The three terminals of Corresponding symbols for these terms are shown in designs apply to OTA circuits. The three terminals of Eigure 28.

Regardless of its depiction, the OTA section has ^a high-input impedance (B-input), ^a low-input/output impedance (E-input), and ^a high-impedance current source output (C-output).

TRANSCONDUCTANCE (OTA) SECTION—AN

circuits—the transistor is also a voltage-controlled the OTA are labeled B, E, and C. This labeling calls attention to its similarity to ^a transistor, yet draws distinction for clarity. While the OTA is similar to ^a transistor, one essential difference is the sense of the C-output current: it flows out the C terminal for positive B-to-E input voltage and in the C terminal for negative B-to-E input voltage. The OTA offers many advantages over ^a discrete transistor. The OTA is self-biased, simplifying the design process and reducing component count. In addition, the OTA is far more linear than a transistor. Transconductance of the OTA is constant over ^a wide range of collector currents—this feature implies ^a fundamental improvement of linearity.

BASIC CONNECTIONS

Figure 29 shows basic connections required for operation. These connections are not shown in **Figure 28. Symbols and Terms** subsequent circuit diagrams. Power-supply bypass capacitors should be located as close as possible to the device pins. Solid tantalum capacitors are generally best.

Figure 29. Basic Connections

Texas **INSTRUMENTS**

QUIESCENT CURRENT CONTROL PIN

The quiescent current of the transconductance portion of the OPA861 is set with a resistor, R_{ADJ} , connected from pin 1 to –V_S. The maximum quiescent current is 6mA. R_{ADJ} should be set between 50Ω and 1kΩ for optimal performance of the OTA section. This range corresponds to the 5mA quiescent current for $R_{ADJ} = 50Ω$, and 1mA for $R_{ADJ} =$ 1kΩ. If the I_o adjust pin is connected to the negative supply, the quiescent current will be set by the 250Ω internal resistor.

Reducing or increasing the quiescent current for the possibilities such as AGC, dynamic control of AC
OTA section controls the bandwidth and AC behavior behavior, or VCO. OTA section controls the bandwidth and AC behavior as well as the transconductance. With $R_{ADJ} = 250\Omega$, this sets approximately 5.4mA total quiescent current at 25°C. It may be appropriate in some applications to trim this resistor to achieve the desired quiescent current or AC performance.

Applications circuits generally do not show the **resistor RQ, but it is required for proper operation.** states—common emitter, common base, and

With a fixed $R_{AD,J}$ resistor, quiescent current increases with temperature (see [Figure](#page-7-0) 11 in the *Typical Characteristics* section). This variation of current with temperature holds the transconductance, g_m , of the OTA relatively constant with temperature (another advantage over ^a transistor).

It is also possible to vary the quiescent current with ^a control signal. The control loop in Figure 30 shows 1/2 of ^a REF200 current source used to develop 100mV on R_1 . The loop forces 125mV to appear on $R₂$. Total quiescent current of the OPA861 is approximately 37 \times I_1 , where I_1 is the current made to flow out of pin 1.

Figure 30. Optional Control Loop for Setting Quiescent Current

With this control loop, quiescent current will be nearly constant with temperature. Since this method differs from the temperature-dependent behavior of the internal current source, other temperature-dependent behavior may differ from that shown in the Typical Characteristics. The circuit of Figure 30 will control the $I₀$ of the OPA861 somewhat more accurately than with a fixed external resistor, R_Q . Otherwise, there is no fundamental advantage to using this more complex biasing circuitry. It does, however, demonstrate the possibility of signal-controlled quiescent current. This capability may suggest other

BASIC APPLICATIONS CIRCUITS

Most applications circuits for the OTA section consist of ^a few basic types, which are best understood by analogy to a transistor. Used in voltage-mode, the
OTA section can operate in three basic operating common collector. In the current-mode, the OTA can be useful for analog computation such as current amplifier, current differentiator, current integrator, and current summer.

Common-E Amplifier or Forward Amplifier

[Figure](#page-13-0) 31 compares the common-emitter configuration for ^a BJT with the common-E amplifier for the OTA section. There are several advantages in using the OTA section in place of ^a BJT in this configuration. Notably, the OTA does not require any biasing, and the transconductance gain remains constant over temperature. The output offset voltage is close to 0, compared with several volts for the common-emitter amplifier.

The gain is set in ^a similar manner as for the BJT equivalent with Equation 1:

$$
G = \frac{R_{L}}{\frac{1}{g_m} + R_{E}}
$$
\n(1)

Just as transistor circuits often use emitter degeneration, OTA circuits may also use degeneration. This option can be used to reduce the effects that offset voltage and offset current might otherwise have on the DC operating point of the OTA. The E-degeneration resistor may be bypassed with ^a large capacitor to maintain high AC gain. Other circumstances may suggest ^a smaller value capacitor used to extend or optimize high-frequency performance.

Figure 31. Common-Emitter vs Common-E Amplifier

The transconductance of the OTA with degeneration can be calculated by Equation 2:

$$
g_{m\deg} = \frac{1}{\frac{1}{g_m} + R_E} \tag{2}
$$

A positive voltage at the B-input, pin 3, causes ^a positive current to flow out of the C-input, pin 8. This gives ^a noninverting gain where the circuit of Figure 31a is inverting. Figure 31b shows an amplifier connection of the OPA861, the equivalent of ^a common-emitter transistor amplifier. Input and output can be ground-referenced without any biasing. The amplifier is non-inverting because of the sense of the output current. **Figure 33. Forward Amplifier Design Equations**

The forward amplifier shown in Figure 32 and Figure 33 corresponds to one of the basic circuits used to characterize the OPA861. Extended characterization of this topology appears in the *Typical Characteristics* section of this datasheet.

www.ti.com **www.ticom** and the set of the set

Common-C Amplifier

Figure 34b shows the OPA861 connected as an E-follower—a voltage buffer. It is interesting to notice that the larger the \bar{R}_E resistor, the closer to unity gain This low impedance can be converted to a high the buffer will be. If the OPA861 is to be used as a buffer, use $R_E \ge 500\Omega$ for best results. For the OPA861 used as ^a buffer, the gain is given by Equation 3:

$$
G = \frac{1}{1 + \frac{1}{g_m \times R_E}} \approx 1
$$
\n(3)

Figure 34. Common-Collector vs Common-C Amplifier

A low value resistor in series with the B-input is recommended. This resistor helps isolate trace parasitic from the inputs, reduces any tendency to oscillate, and controls frequency response peaking. Typical resistor values are from 25Ω to 200Ω.

Common-B Amplifier

Figure 35 shows the Common-B amplifier. This configuration produces an inverting gain and a low impedance input. Equation 4 shows the gain for this configuration.

$$
G = \frac{R_{L}}{R_{E} + \frac{1}{g_{m}}} \approx -\frac{R_{L}}{R_{E}}
$$
\n(4)

impedance by inserting the buffer amplifier in series.

Current-Mode Analog Computations

As mentioned earlier, the OPA861 can be used advantageously for analog computation. Among the application possibilities are functionality as ^a current amplifier, current differentiator, current integrator, current summer, and weighted current summer. [Table](#page-15-0) 1 lists these different uses with the associated transfer functions.

These functions can easily be combined to form active filters. Some examples using these current-mode functions are shown later in this document.

Figure 35. Common-Base Transistor vs

FXAS INSTRUMENTS

SBOS338E–AUGUST 2005–REVISED AUGUST 2008.. **www.ti.com**

OPA861 APPLICATIONS

Control-Loop Amplifier DC-Restore Circuit

A new type of control loop amplifier for fast and The OPA861 can be used advantageously with an precise control circuits can be designed with the operational amplifier, here the OPA656, as ^a OPA861. The circuit of [Figure](#page-16-0) 36 illustrates a series DC-restore circuit. Figure 37 illustrates this design. connection of two voltage control current sources that Depending on the collector current of the have an integral (and at higher frequencies, ^a transconductance amplifier (OTA) of the OPA861, ^a proportional) behavior versus frequency. The control switching function is realized with the diodes D_1 and loop amplifiers show an integrator behavior from DC D_2 . to the frequency represented by the RC time constant of the network from the C-output to GND. Above this frequency, they operate as an amp with constant gain. The series connection increases the overall gain to about 110dB and thus minimizes the control loop deviation. The differential configuration at the inputs The condition to charge C_1 is set by the voltage enables one to apply the measured output signal and difference between V_{DEF} and V_{OUT} . For the OTA enables one to apply the measured output signal and difference between V_{REF} and V_{OUT} . For the OTA the reference voltage to two identical high-impedance C-output to source current. V_{DEF} has to be greater inputs. The output buffer decouples the C-output of than V_{OUT} . The rate of charge of C₁ is set by both R₁ the second OTA in order to insure the AC and C₁. The discharge rate is given by R₂ and C₁. performance and to drive subsequent output stages.

When the C-output is sourcing current, the capacitor C_1 is being charged. When the C-output is sinking current, D_1 is turned off and D_2 is turned on, letting the voltage across C_1 be discharged through R_2 .

C-output to source current, V_{REF} has to be greater and C_1 . The discharge rate is given by R_2 and C_1 .

Figure 37. DC Restorer Circuit

Negative Impedance Converter Filter: Low-Pass

The OPA861 can be used as ^a negative impedance converter to realize the low-pass filer shown in Figure 38.

Figure 38. Low-Pass Negative Impedance Converter Filter

The transfer function is shown in Equation 5:

$$
\frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{1}{1 + sC_2R + s^2C_1C_2R^2}
$$
(5)

with:

$$
\omega_0 = \frac{1}{\sqrt{C_1 C_2} R}
$$

$$
Q = \sqrt{\frac{C_1}{C_2}}
$$

SBOS338E–AUGUST 2005–REVISED AUGUST 2008.. **www.ti.com**

The input impedance is shown in Equation 6:

$$
Z_{IN} = \frac{1}{2sC} + R\frac{1 + sRC}{1 + 2sRC}
$$
 (6)

Figure 39 shows the frequency responses for low-pass, Butterworth filters set at 20kHz and 10MHz.

 $C_1 = \frac{1}{2}$ $\frac{1}{2} \times C_2 = 5.6 \mu F$. For the 10MHz filter, the For the 20kHz filter, set R to 1K Ω and parasitic capacitance at the output pin needs to be have otherwise occured in the resistive network. taken into consideration. In the example of Figure 39, the parasitic is 3pF, which gives us the settings of R = 1.13kΩ, C₁ = 10pF, and C₂ = 17pF.

Figure 39. Small-Signal Frequency Response for ^a Figure 40. Differential Driver Common-Mode Low-Pass Negative Impedance Converter Filter

Differential Line Driver/Receiver

The wide bandwidth and high slew rate of the OPA861 current-mode amplifier make it an ideal line driver. The circuit in Figure 41 makes use of two OPA861s to realize ^a single-ended to differential conversion. The high-impedance current source
output of the OPA861 allows it to drive low-impedance or capacitive loads without series resistances and avoids any attenuation that would

The OPA861 used as a differential receiver exhibits excellent common-mode rejection ratio, as can be seen in Figure 40.

Figure 41. Twisted-Pair Differential Driver and Receiver with the OPA861

ACTIVE FILTERS USING THE OPA861 IN

One further example of the versatility of the Diamond Transistor and Buffer is the construction of high-frequency (> 10MHz) active filters. Here, the Current Conveyor structure, shown in Figure 42, is used with the Diamond Transistor as a Current Conveyor.

The method of converting RC circuit loops with quite close to an ideal current amplifier. The operational amplifiers in Current Conveyor structures well-known Sallen-Key low-pass filter with positive operational amplifiers in Current Conveyor structures well-known Sallen-Key low-pass filter with positive
is based upon the adjoint network concept. A network feedback, is an example of conversion into is based upon the adjoint network concept. A network feedback, is an example of conversion into
is reversible or reciprocal when the transfer function Current-Conveyor structure, see Figure 45. The is reversible or reciprocal when the transfer function Current-Conveyor structure, see [Figure](#page-20-0) 45. The does not change even when the input and output positive gain of the operational amplifier becomes a does not change even when the input and output positive gain of the operational amplifier becomes a
have been exchanged. Most networks, of course, are energative second type of Current Conveyor (CCII), as have been exchanged. Most networks, of course, are energative second type of Current Conveyor (CCII), as nonreciprocal. The networks of Figure 43, perform shown in Figure 42. Both arrangements have nonreciprocal. The networks of [Figure](#page-19-0) 43, perform shown in Figure 42. Both arrangements have

interreciprocally when the input and output are sudentical transfer functions and the same level of interreciprocally when the input and output are identical transfer functions and the same level of exchanged, while the original network. N. is sensitivity to deviations. The most recent exchanged, while the original network, N, is sensitivity to deviations. The most recent exchanged for a new network N, In this case the implementation of active filters in a Current-Convevor exchanged for a new network N_A. In this case, the implementation of active filters in a Current-Conveyor transfer function remains the same, and N_A is the structure produced a second-order Bi-Quad filter. The adjoing network. It is easy to construct an adjoint value of the resistance in the emitter of the Diamond
network for any given circuit, and these networks are Transistor controls the filter characteristic. For more network for any given circuit, and these networks are Transistor controls the filter characteristic. For more
the base for circuits in Current-Convevor structure. information, refer to application note SBOS047, New the base for circuits in Current-Conveyor structure. information, refer to application note [SBOS047](http://www-s.ti.com/sc/techlit/SBOS047), *New* Individual elements can be interchanged according to the list in [Figure](#page-19-0) 44. Voltage sources at the input become short circuits, and the current flowing there becomes the output variable. In contrast, the voltage

output becomes the input, which is excitated by ^a **CURRENT CONVEYOR STRUCTURE** current source. The following equation describes the interreciprocal features of the circuit: $V_{\text{OUT}}/V_{\text{IN}}$ = I_{OUT}/I_{IN}. Resistances and capacitances remain unchanged. In the final step, the operational amplifier with infinite input impedance and 0Ω output impedance is transformed into ^a current amplifier with $0Ω$ input impedance and infinite output impedance. A Diamond Transistor with the base at ground comes

Figure 42. Current Conveyor

Figure 43. Networks

Figure 44. Individual Elements in the Current Conveyor

Figure 45. Universal Active Filter

Transfer Function

The transfer function of the universal active filter of Figure 45 is shown in Equation 7.

$$
F(p) = \frac{V_{OUT}}{V_{IN}} = \frac{s^2 C_1 C_2 R_{1M} \frac{R_{2M}}{R_3} + sC_1 \frac{R_{1M}}{R_2} + \frac{1}{R_1}}{s^2 C_1 C_2 R_{1M} \frac{R_{2M}}{R_{3S}} + sC_1 \frac{R_{1M}}{R_{2S}} + \frac{1}{R_{1S}}}
$$
(7)

Filter Characteristics

Five filter types can be made with this structure:

- For a low-pass filter, set $R_2 = R_3 = \infty$,
- •For a high-pass filter, set $R_1 = R_2 = \infty$,
- •For a bandpass filter, set $R_1 = R_3 = \infty$,
- •For a band rejection filter, set $R_2 = \infty$; $R_1 = R_3$,
- •For an all-pass filter, set $R_1 = R_{1S}$; $R_2 = R_{2S}$; and $R_3 = R_{3S}$.

A few designs for ^a low-pass filter are shown in Figure 46 and Table 2.

Table 2. Component Values for Filters Shown In Figure 46

Figure 46. Butterworth Low-Pass Filter with the Universal Active Filter

The advantages of building active filters using ^a Current Conveyor structure are:

- • The increase in output resistance of operational amplifiers at high frequencies makes it difficult to construct feedback filter structures (decrease in for **B** α **C** α **C**
- • All filter coefficients are represented by resistances, making it possible to adjust the filter frequency response without affecting the filter coefficients.
- • The capacitors which determine the frequency are located between the ground and the current source outputs and are thus grounded on one side. Therefore, all parasitic capacitances can be viewed as part of these capacitors, making them easier to comprehend.
- • The features which determine the frequency characteristics are currents, which charge the integration capacitors. This situation is similar to the transfer characteristic of the Diamond Transistor.

High-CMRR, Moderate Precision, Differential I/O ADC Driver

The circuit shown in Figure 47 depicts an ADC driver implemented with two OPA861s. Since the gain is set here by the ratio of the internal 600Ω resistors and R_F , its accuracy will only be as good as the input resistor of the ADS5272. The small-signal frequency response for this circuit has 150MHz at –3dB bandwidth for ^a gain of approximately 5.6dB, as shown in Figure 48. The advantage of this circuit lies in its high CMRR to 100kHz, as shown in Figure 49. This circuit also has more than 10 bits of linearity.

Figure 47. High CMRR, Moderate Precision, Differential I/O ADC Driver

Figure 48. ADC Driver, Small-Signal Frequency Response

Figure 49. CMRR of the ADC Driver

INSTRUMENTS

Texas

Texas **INSTRUMENTS**

www.ti.com **www.ticom** and the set of the set

DESIGN-IN TOOLS

DEMONSTRATION BOARDS

A printed circuit board (PCB) is available to assist in terms shown in Figure 50. the initial evaluation of circuit performance using the OPA861. This module is available free, as an unpopulated PCB delivered with descriptive documentation. The summary information for the board is shown below:

The board can be requested on the Texas Instruments web site [\(www.ti.com\)](http://www.ti.com).

MACROMODELS AND APPLICATIONS

Computer simulation of circuit performance using SPICE is often useful when analyzing the performance of analog circuits and systems. This principle is particularly true for Video and RF amplifier circuits where parasitic capacitance and inductance can have ^a major effect on circuit performance. A SPICE model for the OPA861 is available through the Texas Instruments web page ([www.ti.com\)](http://www.ti.com). These models do ^a good job of predicting small-signal AC and transient performance under a wide variety of Note that it is the power in the output stage and not operating conditions. They do not do as well in into the load that determines internal power operating conditions. They do not do as well in into the loredicting the harmonic distortion. These models do dissipation. predicting the harmonic distortion. These models do not attempt to distinguish between the package types in their small-signal AC performance.

NOISE PERFORMANCE

The OTA noise model consists of three elements: a voltage noise on the B-input; ^a current noise on the B-input; and ^a current noise on the E-input. Figure 50 shows the OTA noise analysis model with all the Maximum $T_{\rm J} = +85^{\circ}C + (0.19W \times 150^{\circ}C/W) = 114^{\circ}C$. noise terms included. In this model, all noise terms are taken to be noise voltage or current density terms in either nV/√Hz or pA/√Hz.

The total output spot noise voltage can be computed as the square root of the sum of all squared output noise voltage contributors. Equation 8 shows the general form for the output noise voltage using the

erms shown in Figure 50.
\n
$$
e_{o} = \sqrt{\left[e_{n}^{2} + (R_{s}i_{bn})^{2} + 4kTR_{s}\right]\left[\frac{R_{L}}{R_{G} + \frac{1}{9m}}\right]^{2} + \left[(R_{s}i_{bi})^{2} + 4kTR_{s}\right]\frac{R_{L}}{\frac{1}{9m}}}
$$
\n(8)

THERMAL ANALYSIS

Maximum desired junction temperature will set the maximum allowed internal power dissipation as described below. In no case should the maximum junction temperature be allowed to exceed 150°C.

Operating junction temperature (T_{J}) is given by $T_A + P_D \times \theta_{JA}$. The total internal power dissipation **SUPPORT SUPPORT EXECUTE:** (P_D) is the sum of quiescent power (P_{DQ}) and additional power dissipated in the output stage (P_{D1}) to deliver output current. Quiescent power is simply the specified no-load supply current times the total supply voltage across the part. P_{DI} will depend on the required output signal and load but would, for the OPA861 be at a maximum when the maximum I_{Ω} is being driven into ^a voltage source that puts the maximum voltage across the output stage. Maximum I_O is 15mA times a 9V maximum across the output.

As a worst-case example, compute the maximum T_{J} using an OPA861IDBV in the circuit of [Figure](#page-13-0) 31b operating at the maximum specified ambient temperature of +85°C and driving ^a –1V voltage

 $P_D = 10V \times 5.4mA + (15mA \times 9V) = 185mW$

Although this is still well below the specified maximum junction temperature, system reliability considerations may require lower tested junction temperatures. The highest possible internal dissipation will occur if the load requires current to be forced into the output for positive output voltages or sourced from the output for negative output voltages. This puts ^a high current through ^a large internal voltage drop in the output transistors.

BOARD LAYOUT GUIDELINES

Achieving optimum performance with ^a high-frequency amplifier like the OPA861 requires careful attention to board layout parasitics and **Figure 50. OTA Noise Analysis Model** external component types. Recommendations that will optimize performance include:

a) Minimize parasitic capacitance to any AC ground **e) Socketing ^a high-speed part like the OPA861 is** for all of the signal I/O pins. Parasitic capacitance on **not recommended.** The additional lead length and the inverting input pin can cause instability: on the pin-to-pin capacitance introduced by the socket can noninverting input, it can react with the source create an extremely troublesome parasitic network impedance to cause unintentional bandlimiting. To that makes it almost impossible to achieve ^a smooth, reduce unwanted capacitance, ^a window around the stable frequency response. Best results are obtained signal I/O pins should be opened in all of the ground by soldering the OPA861 onto the board. and power planes around those pins. Otherwise, ground and power planes should be unbroken elsewhere on the board.

b) Minimize the distance (< 0.25") from the complementary bipolar process. The internal junction power-supply pins to high-frequency 0.1μ F breakdown voltages are relatively low for these very decoupling capacitors. At the device pins, the ground small geometry devices. These breakdowns are decoupling capacitors. At the device pins, the ground small geometry devices. These breakdowns are and power-plane layout should not be in close reflected in the Absolute Maximum Ratings table. All and power-plane layout should not be in close reflected in the *Absolute Maximum Ratings* table. All proximity to the signal I/O pins. Avoid narrow power device pins are protected with internal ESD protection and ground traces to minimize inductance between diodes to the power supplies as shown in Figure 51. the pins and the decoupling capacitors. The power-supply connections should always be decoupled with these capacitors. An optional supply decoupling capacitor (0.1µF) across the two power supplies (for bipolar operation) will improve 2nd-harmonic distortion performance. Larger (2.2µF to 6.8µF) decoupling capacitors, effective at lower frequency, should also be used on the main supply pins. These may be placed somewhat farther from the device and may be shared among several devices in the same area of the PC board. **Figure 51. Internal ESD Protection**

c) Careful selection and placement of external components will preserve the high-frequency These diodes provide moderate protection to input **performance of the OPA861.** Resistors should be a overdrive voltages above the supplies as well. The **performance of the OPA861.** Resistors should be a soverdrive voltages above the supplies as well. The very low reactance type. Surface-mount resistors protection diodes can typically support 30mA very low reactance type. Surface-mount resistors beta protection diodes can typically support 30mA
work best and allow a tighter overall layout. Metal film continuous current. Where higher currents are work best and allow a tighter overall layout. Metal film continuous current. Where higher currents are or carbon composition, axially-leaded resistors can possible (for example, in systems with ±15V supply or carbon composition, axially-leaded resistors can bossible (for example, in systems with ±15V supply also provide good high-frequency performance. parts driving into the OPA861), current-limiting series also provide good high-frequency performance. parts driving into the OPA861), current-limiting series Again, keep
Again, keep their leads and PC board traces as short resistors should be added into the two inputs. Keep Again, keep their leads and PC board traces as short resistors should be added into the two inputs. Keep
as possible. Never use wirewound type resistors in a these resistor values as low as possible since high as possible. Never use wirewound type resistors in a high-frequency application.

d) Connections to other wideband devices on the board may be made with short, direct traces or through onboard transmission lines. For short connections, consider the trace and the input to the next device as ^a lumped capacitive load. Relatively wide traces (50mils to 100mils) should be used, preferably with ground and power planes opened up around them.

INPUT AND ESD PROTECTION

The OPA861 is built using ^a very high-speed diodes to the power supplies as shown in Figure 51.

values degrade both noise performance and frequency response.

Page

Page

www.ti.com

SBOS338E-AUGUST 2005-REVISED AUGUST 2008

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Revision D (August 2006) to Revision E

Changed storage temperature range rating in Absolute Maximum Ratings table from -40°C to +125°C to -65°C to

Changes from Revision C (June 2006) to Revision D

IMENTS

PACKAGING INFORMATION

(1) The marketing status values are defined as follows:

ACTIVE: Product device recommended for new designs.

LIFEBUY: TI has announced that the device will be discontinued, and a lifetime-buy period is in effect.

NRND: Not recommended for new designs. Device is in production to support existing customers, but TI does not recommend using this part in a new design.

PREVIEW: Device has been announced but is not in production. Samples may or may not be available.

OBSOLETE: TI has discontinued the production of the device.

(2) Eco Plan - The planned eco-friendly classification: Pb-Free (RoHS), Pb-Free (RoHS Exempt), or Green (RoHS & no Sb/Br) - please check <http://www.ti.com/productcontent> for the latest availability information and additional product content details. **TBD:** The Pb-Free/Green conversion plan has not been defined.

Pb-Free (RoHS): TI's terms "Lead-Free" or "Pb-Free" mean semiconductor products that are compatible with the current RoHS requirements for all 6 substances, including the requirement that lead not exceed 0.1% by weight in homogeneous materials. Where designed to be soldered at high temperatures, TI Pb-Free products are suitable for use in specified lead-free processes.

Pb-Free (RoHS Exempt): This component has a RoHS exemption for either 1) lead-based flip-chip solder bumps used between the die and package, or 2) lead-based die adhesive used between the die and leadframe. The component is otherwise considered Pb-Free (RoHS compatible) as defined above.

Green (RoHS & no Sb/Br): TI defines "Green" to mean Pb-Free (RoHS compatible), and free of Bromine (Br) and Antimony (Sb) based flame retardants (Br or Sb do not exceed 0.1% by weight in homogeneous material)

(3) MSL, Peak Temp. -- The Moisture Sensitivity Level rating according to the JEDEC industry standard classifications, and peak solder temperature.

Important Information and Disclaimer:The information provided on this page represents TI's knowledge and belief as of the date that it is provided. TI bases its knowledge and belief on information provided by third parties, and makes no representation or warranty as to the accuracy of such information. Efforts are underway to better integrate information from third parties. TI has taken and continues to take reasonable steps to provide representative and accurate information but may not have conducted destructive testing or chemical analysis on incoming materials and chemicals. TI and TI suppliers consider certain information to be proprietary, and thus CAS numbers and other limited information may not be available for release.

In no event shall TI's liability arising out of such information exceed the total purchase price of the TI part(s) at issue in this document sold by TI to Customer on an annual basis.

TEXAS TRUMENTS www.ti.com 6-Nov-2008

TAPE AND REEL INFORMATION

QUADRANT ASSIGNMENTS FOR PIN 1 ORIENTATION IN TAPE

PACKAGE MATERIALS INFORMATION

*All dimensions are nominal

DBV (R-PDSO-G6)

PLASTIC SMALL-OUTLINE PACKAGE

- NOTES:
	- А. All linear dimensions are in millimeters. This drawing is subject to change without notice. **B.**
	- Body dimensions do not include mold flash or protrusion. Mold flash and protrusion shall not exceed 0.15 per side. $\mathbb{C}.$
	- D. Leads 1,2,3 may be wider than leads 4,5,6 for package orientation.
	- $\underline{\mathbb{E}}$ Falls within JEDEC MO-178 Variation AB, except minimum lead width.

 $D (R-PDSO-G8)$

PLASTIC SMALL-OUTLINE PACKAGE

NOTES: A. All linear dimensions are in inches (millimeters).

B. This drawing is subject to change without notice.

6 Body length does not include mold flash, protrusions, or gate burrs. Mold flash, protrusions, or gate burrs shall not exceed .006 (0,15) per end.

 $\hat{\mathbb{D}}$ Body width does not include interlead flash. Interlead flash shall not exceed .017 (0,43) per side.

E. Reference JEDEC MS-012 variation AA.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute ^a license from TI to use such products or services or ^a warranty or endorsement thereof. Use of such information may require ^a license from ^a third party under the patents or other intellectual property of the third party, or ^a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where ^a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2008, Texas Instruments Incorporated